



## BRAC UNIVERSITY

CSE 350: Digital Electronics and Pulse techniques

Exp-01: Implementing Diode Logic (DL) gates

Name: Ms Rodry Tahmid	Section: 10
ID: 20101024	Group: 2

### Objectives

1. Construct Diode Logic (DL) gates.
2. Understanding the circuit operations.

### Equipment and component list

#### *Equipment*

1. Digital Multimeter
2. DC power supply

#### *Component*

- NPN Transistor (C828) - x1 piece
- Diode 1N4003 - x2 pieces
- Resistors -
  - ◆ 450  $\Omega$  - x2 piece
  - ◆ 15 K $\Omega$  - x1 piece
  - ◆ 2.2 K $\Omega$  - x1 piece
  - ◆ 100 K $\Omega$  - x1 piece

 


Fig 1: OR gate

 


Fig 2: AND gate

## Task-01: OR gate

### THEORY

In digital logic, a 2-input OR gate outputs a logical HIGH if at least one of the inputs is HIGH. Otherwise, the output of the OR gate is logical LOW.

In this task, we will implement a Diode Logic (DL) OR gate. In Fig. 1, we can see two input nodes (A and B) and one output node (Y) of the OR gate. We will consider 5V as logical HIGH input and 0V as logical LOW input in our experiment. Now, if any of the inputs are set to 5V, the corresponding diode is turned on. As a result, a current flows through that diode. This current ultimately flows through  $R$  towards the ground, thus creating a voltage drop across the  $R$  resistor. As  $R_1$  and  $R_2$  resistors are very small compared to  $R$ , the voltage drop across  $R$  will be close to 5V. In this case, we will consider the obtained output voltage at node Y to be logically HIGH. Next, if all the inputs are set to 0V, no current flows through the diodes and resistor  $R$ . As a result, the voltage drop across  $R$  will be zero. So, the output voltage will be 0V, which we will consider to be logically LOW.

## Task-02: AND gate

### THEORY

In digital logic, a 2-input AND gate outputs a logical LOW if at least one of the inputs is LOW. Otherwise, the output of the AND gate is logical HIGH.

Similar to the previous task, we will implement a Diode Logic (DL) AND gate. If any of the inputs are set to 0V, the corresponding diode is turned on. As a result, a current flows through that diode from the  $V_R$  voltage source. This current flows through  $R$  and creates a voltage drop across the resistor. As  $R_1$  and  $R_2$  resistors are very small compared to  $R$ , the voltage drop across  $R$  will be close to 5V. As a result, the obtained output voltage at node Y will be close to 0V which we will consider as logically LOW. Next, if all the inputs are set to 5V, no current flows through the diodes and resistor  $R$ . Therefore, the voltage drop across  $R$  will be zero. So, the output voltage will be the same as  $V_R$  or 5V, which is logically HIGH.

## Task-03: Inverter (NOT gate)

### THEORY

In digital logic, an inverter or NOT gate is a logic gate which implements logical negation. It has a single input and a single output where the output is the exact opposite of the input. Meaning, if the input is Logical High, the output will be Logical Low and vice versa. The RTL implementation of an inverter circuit is shown in Figure 03.

Here the input is applied to the base of a Transistor or, BJT ( $Q_1$ ) through the resistor  $R_1$  and the output is available at the collector terminal (point Y). We connect the ground terminal to the emitter node directly and to the base node through the resistor  $R_2$ . Hence, when the input  $V_i$  is LOW (0V), the 'Base' terminal

$$4.33 = 5 - V_B.$$

$$V_{F1} = V_i - V_B.$$

$$R_c = 2.18 k\Omega$$

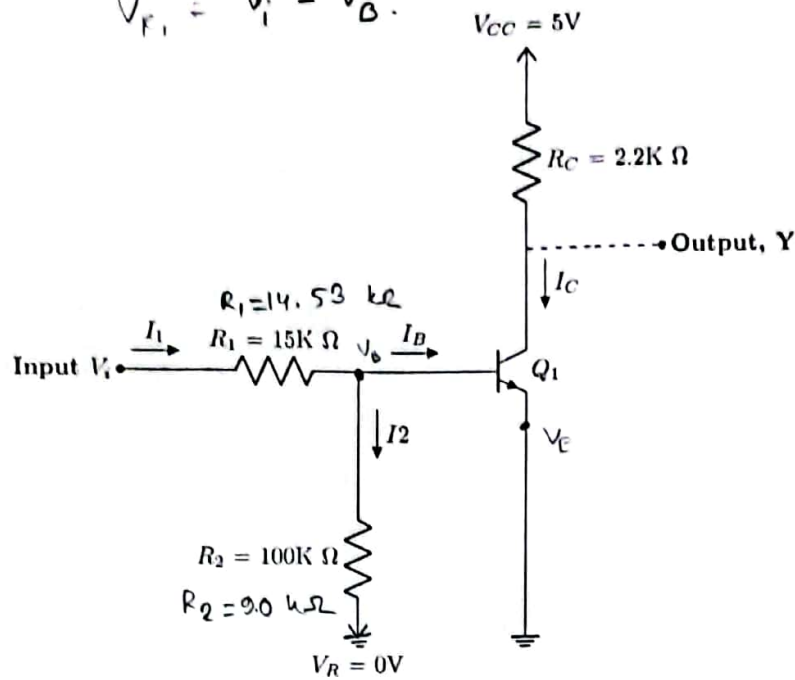


Fig 3: Inverter (NOT gate)

of the transistor cannot be at a voltage higher than zero. For  $Q_1$  to be turned ON, the Base-Emitter voltage difference must be greater than 0.5V. Thus, the BJT cannot turn ON when the input is LOW and operates in cutoff mode. This means  $Q_1$  acts like an open circuit and the current passing through the  $R_C$  resistor ( $I_C$ ) is zero. As a result, there will be no voltage drop in the resistor  $R_C$  and the voltage of the output point (Y) will be same as  $V_{CC} = 5V$  (High).

On the other hand, if a HIGH input (5V) is applied at the input terminal ( $V_i$ ),  $Q_1$  will be driven into saturation mode. In this mode, the Collector-Emitter voltage difference ( $V_{CE}$ ) is nearly 0.2V. As the emitter is connected to the ground terminal, the emitter voltage ( $V_E$ ) is zero. Hence, the collector voltage will be close to 0.2V (LOW). Thus, the output of the circuit is always the opposite of the input.

### Procedure:

1. Connect the circuit as shown in Fig: 1, 2 & 3.
2. Observe the output for all possible input combinations thus verify the type of gate.
3. Fill up the following tables for OR gate, AND gate and Inverter.

## Data Tables

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	0	0	0	0	0
0	5	0	$21.9 \times 10^{-3}$	0	$4.86 \times 10^{-5}$	4.55
5	0	$21.7 \times 10^{-3}$	0	$4.83 \times 10^{-5}$	0	4.55
5	5	$11.6 \times 10^{-3}$	$10.6 \times 10^{-3}$	$2.58 \times 10^{-5}$	$2.36 \times 10^{-5}$	4.59

Table 1: Table for OR Gate

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	$11.4 \times 10^{-3}$	$10.5 \times 10^{-3}$	$2.53 \times 10^{-5}$	$2.33 \times 10^{-5}$	0.425
0	5	$21.7 \times 10^{-3}$	0	$4.83 \times 10^{-5}$	0	0.36
5	0	0	$21.9 \times 10^{-3}$	0	$4.87 \times 10^{-5}$	0.467
5	5	0	0	0	0	4.97

Table 2: Table for AND Gate

$V_i$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)	$V_{RC}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$I_B$ (mA)	$I_C$ (mA)	$V_Y$ (V)
0	0	0	0	0	0	0	0	5.02
5	<u>4.33</u>	<u>0.681</u>	<u>4.97</u>	0.298	<u><math>7.57 \times 10^{-3}</math></u>	0.29043	2.28	$37.6 \times 10^{-3}$

Table 3: Table for RTL inverter



## Report

$$\text{Let, } \beta_{\text{forward}} = 10$$

Please answer the following questions briefly in the given space.

1. Verify that the transistor will be operating in the saturation and cutoff region in two cases for the inverter circuit (Use experimental data for verification).

Ans. When  $V_{in} = 0$  (low)

$$I_B = 0, V_o = 5.02 \text{ (high)}$$

↓  
Transistor is  
in cutoff region  
(verified)

When  $V_{in} = 5$  (high)

$$\beta_{\text{forced}} = \frac{I_c}{I_B} < \beta_{\text{forward}}$$

$$\beta_{\text{forced}} = \frac{2.28}{0.29043} = 7.85$$

$$7.85 < 10$$

$$\beta_{\text{forced}} < \beta_{\text{forward}} \text{ (verified)}$$

2. For OR gate circuit, should  $I_{R_1}$  and  $I_{R_2}$  be equal theoretically when  $V_A = V_B = 5V$ ? Did you obtain a similar result in your experiment? Explain briefly.

Ans. When  $V_A = V_B = 5V$  [Case-3: Both high],  $I_{R_1}$  &  $I_{R_2}$  should be

equal theoretically. Yes, we obtained a similar result in our experiment where  $I_{R_1} = 2.58 \times 10^{-5} \text{ mA}$  and  $I_{R_2} = 2.36 \times 10^{-5} \text{ mA}$ . So,  $I_{R_1} \approx I_{R_2}$ . The slight  $0.0000022 \text{ mA}$  difference is the absolute error occurred due to the different  $V_{R_1}$ ,  $V_{R_2}$  values from which  $I_{R_1}$  and  $I_{R_2}$  were calculated.  $V_{R_1}$  and  $V_{R_2}$  have slight different values because they were measured using a multimeter and we all know that multimeters show the values within a range and not the exact values.

3. (For both OR AND gate circuits) Will the diodes  $D_1$  and  $D_2$  work, if  $V_A = V_B = 6V$  and  $V_R = 5V$ ?

Ans. If  $V_A = V_B = 6V$  [Case-3: Both inputs high] and  $V_R = 5V$ :

For OR gate circuit, the diodes  $D_1$  and  $D_2$  will work because

$$I_A = I_B = \frac{6-5}{450} = 2.2 \times 10^{-3} \text{ A} > 2.644 \times 10^{-5} \text{ A}, \text{ which}$$

it was supposed to be if  $[V_R = V_{R_1} = V_{R_2}]$   $V_R$  wasn't constant.


For AND gate circuit, since both the inputs are high and the diodes are in reverse direction, there will be no current flow across the diodes and the diodes will act as open circuits and  $V_y = V_R = 5V$ . So, the<sup>5</sup> diodes will be off i.e. will not work.

4. What is the function of  $V_R = 0V$  at the base of an inverter in figure 3?

Ans.

$V_R = 0$  Voltage means the  $R_2$  resistor is basically grounded. Its function is to expand the very small transistor input voltage range (about  $0.7V$ ) to the logical "1" level (about  $5V$ ) by converting the input voltage into current. The base resistor's ( $R_2$ 's) resistance is settled by a compromise: it is chosen low enough to saturate the transistor and high enough to obtain high input resistance.

5. Assuming AND gate, Draw the output.

 


AND gate

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Ans.

	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$
A	1	0	0	1	0	0	1	1
B	1	1	0	0	1	0	0	0
Output Y	1	0	0	0	0	0	0	0

 

## Data Tables

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	0	0	0	0	0
0	5	0	$21.9 \times 10^{-3}$	0	$4.86 \times 10^{-5}$	4.55
5	0	$21.7 \times 10^{-3}$	0	$4.83 \times 10^{-5}$	0	4.55
5	5	$11.6 \times 10^{-3}$	$10.6 \times 10^{-3}$	$2.58 \times 10^{-5}$	$2.34 \times 10^{-5}$	4.59

Table 4: Table for OR Gate

$V_A(V)$	$V_B(V)$	$V_{R1}(V)$	$V_{R2}(V)$	$I_{R1}(mA)$	$I_{R2}(mA)$	$V_Y(V)$
0	0	$11.4 \times 10^{-3}$	$10.5 \times 10^{-3}$	$1.53 \times 10^{-5}$	$2.33 \times 10^{-5}$	0.425
0	5	$21.7 \times 10^{-3}$	0	$4.83 \times 10^{-5}$	0	0.36
5	0	0	$21.9 \times 10^{-3}$	0	$4.87 \times 10^{-5}$	0.467
5	5	0	0	0	0	4.97

Table 5: Table for AND Gate

$V_i$ (V)	$V_{R1}$ (V)	$V_{R2}$ (V)	$V_{RC}$ (V)	$I_1$ (mA)	$I_2$ (mA)	$I_B$ (mA)	$I_C$ (mA)	$V_Y$ (V)
0	0	0	0	0	0	0	0	5.02
5	4.35	0.681	4.97	0.298	$7.57 \times 10^{-3}$	0.29043	2.28	$37.6 \times 10^{-3}$

Table 6: Table for RTL inverter

*Sayac*  
Signature



### Team Members:

- ① Ms Rodsy Tahmid Id: 20101021
- ② Israt Jahan Ayshi Id: 20101618
- ③ Tasnia Zaman Priya Id: 20301296
- ④ Bousra Jahan Lia
- ⑤ Abir Islam

Performance Date: 06 Oct 2022

Submission Date: 13 Oct 2022